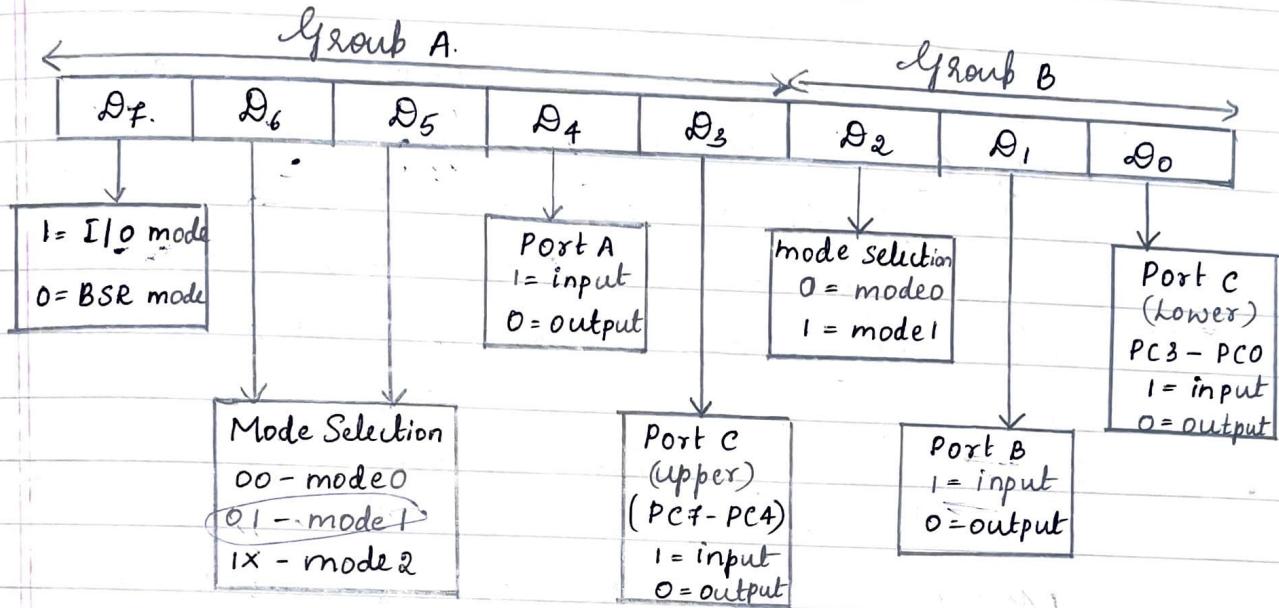


Module - 5
Interfacing

Date / Page

55

Q1 Explain control word format of 8255. (I/O mode of 8255) [Jan 2018 / July 2018 (6M)]



8255 control word format (I/O mode)

- Control word format also called I/O selector. is used to select I/O mode for 8255
- Intel calls mode 0 as the basic I/O mode.
- In mode 0, any port such as A, B or C can be programmed as input or output.
- A given port cannot be input/output at the same time.
- 8255 can be programmed in any of the 4-modes, by sending a byte to the control register of 8255.
- To find the address of each of ports A, B, C & control register we use the method called as "mapping" the I/O port.

Jan 2018 (8M)

56

Q) Explain the various modes of 8255 & find the control word for the following.

- ⇒ i) All ports of A, B, & C are OPP ports (mode)
ii) PA=IN, PB=OUT, PCL=OUT & PCH=OUT

→ Various modes of 8255 :- mode 0, 1, 2 & BSR


- i) Mode 0 :- i) It is also called as simple I/O mode.
ii) In this mode any ports like, A, B, C & Control register can be used as input or output.
iii) In this mode, either all bits are out or all bits are in.
iv) Most of the applications involving 8255, use mode 0.

- 2) Mode 1 :- i) In this port A & port B can be used as input / output port with handshaking capabilities.
ii) Handshaking capabilities are provided by the bits of port C.

- 3) Mode 2 :- i) In this mode port A can be used as bidirectional I/O port with handshaking capabilities, provided by port C.
ii) Port B can be used as simple I/O mode or handshaking mode.

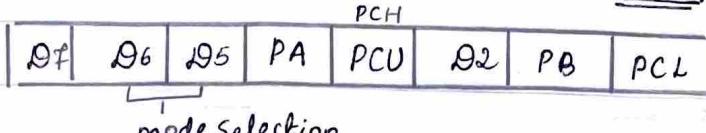- 4) BSR (bit set / reset) mode :- i) In this mode only the individuals bits of port C can be programmed.
ii) It can be also used for enabling / disabling interrupt.


→ i) All ports of A, B, C are o/p ports mode 0.



1	0	0	0	0	0	0	0
---	---	---	---	---	---	---	---

 $= 10000000_2 = 80h$

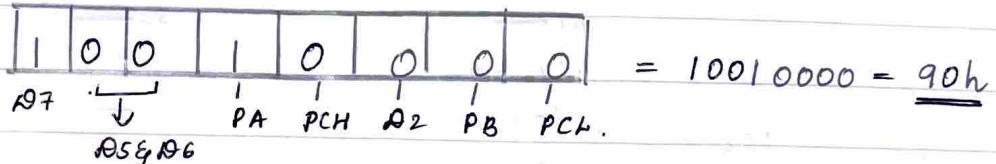ii) PA = in, PB = out, PCL = out, PCH - out mode 0




3) Explain the features of 8255.

features of 8255 are:-

- 8255A is a widely used, programmable, parallel I/O device.
- It is compatible with all Intel and most other microprocessors.
- It is completely TTL compatible.
- It has three 8 bit ports: port A, B & C, which are arranged in three groups of 24 pins.
- 8255 can operate in 3 I/O modes: i) mode 0 ii) mode 1 iii) mode 2
- It can be programmed to transfer data under various conditions, from simple I/O to interrupt I/O.
- Its BSR mode allows to set/reset the bits of port C.
- All I/O pins of 8255 has 2.5 mA DC driving capacity.

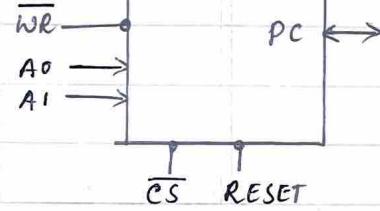4. Draw the pin diagram of 8255 chip & explain the signals.



PA ₃	1	40	PA ₄
PA ₂	2	39	PA ₅
PA ₁	3	38	PA ₆
PA ₀	4	37	PA ₇
RD	5	36	WR
CS	6	35	RSET
GND _A	7	8	
A ₁	8	2	D ₀
A ₀	9	5	D ₁
PCF	10	34	D ₂
PC6	11	33	D ₃
PC5	12	32	D ₄
PC9	13	31	D ₅
PC0	14	30	D ₆
PC1	15	29	D ₇
PC2	16	28	
PC3	17	27	VCC (+5V)
PB0	18	26	PB ₇
PB1	19	25	PB ₆
PB2	20	24	PB ₅
		23	PB ₄
		22	PB ₃

Pin diagram of 8255.

PA₀-PA₇ (port A) :- There are 8 bit I/o port pins of port A, used to send data to the output device and to receive the data from input device.

PB₀-PB₇ (port B) :- There are 8 bit I/o (bidirectional) pins of port B, used to send data to the o/p device & receive data from the i/p device.

PC0- PCF (port C) :- These 8 bit directional I/o pins of port C can be further divided

into 2 groups: PCL and PCU. These groups can individually transfer data in or out when programmed for simple I/O.

RD and WR :- These 2 active-low control signals are inputs to the 8255. Using this pins CPU can read / write data on the ports.

A0 and A1 :- Along with RD & WR, these A0 & A1 signals control the selection of control / status word registers.

CS (chip select) :- This is an active low input which can be used for data transfer operation b/w CPU & 8255.


D₀ - D₇ (databus) :- These bidirectional, tri-state databus lines are connected to system databus.

RESET :- This is an active high input into 8255. It is used to clear the control register & all ports are initialized as input ports.


A1	A0	RD	WR	CS	operation
input operation (read)					
0	0	0	1	0	Port A to databus
0	1	0	1	0	Port B to databus
1	0	0	1	0	Port C to databus
Output operation (write)					
0	0	1	0	0	databus to port A
0	1	1	0	0	" port B
1	0	1	0	0	" port C
1	1	1	0	0	control register
Disable function					
X	X	X	X	1	data bus tri state
1	1	0	1	0	Illegal condition
X	X	1	1	0	data bus tri state

5) Explain the steps to interface the 8051 microcontroller

ADC 0808 to
(ADC 0809)

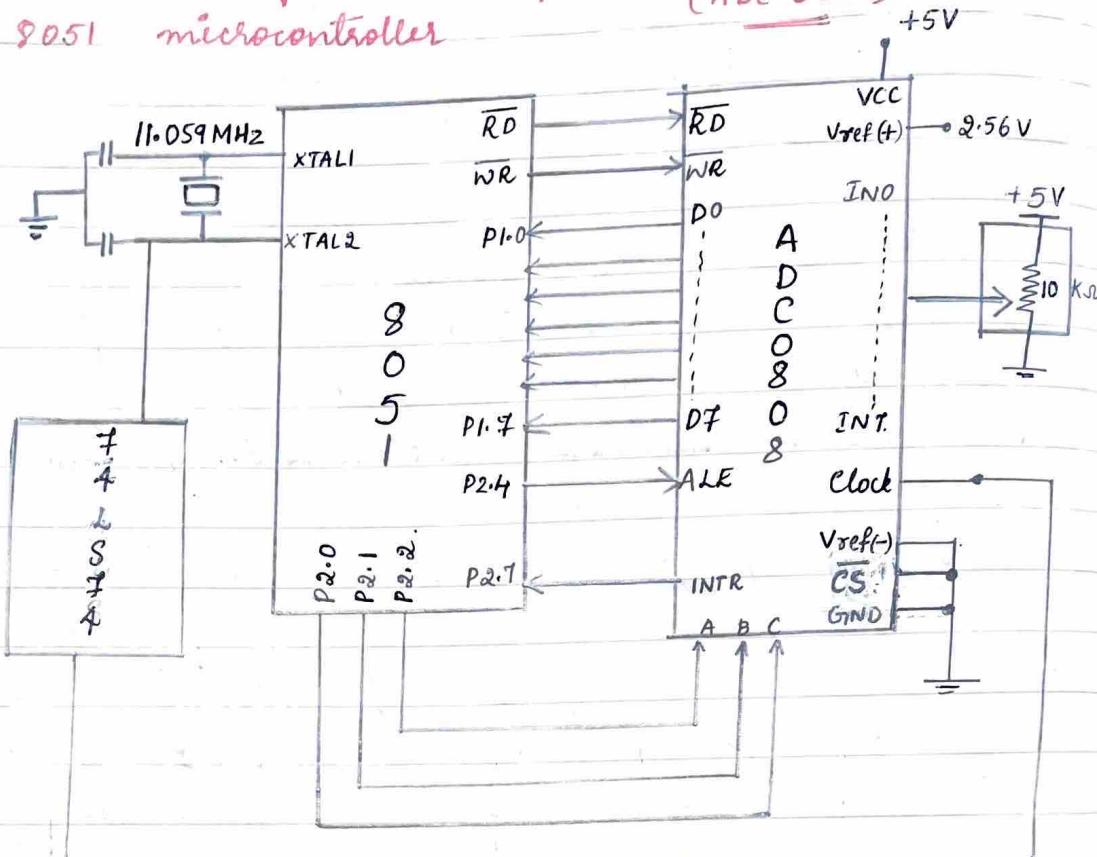

ADC 0808 interfacing with 8051

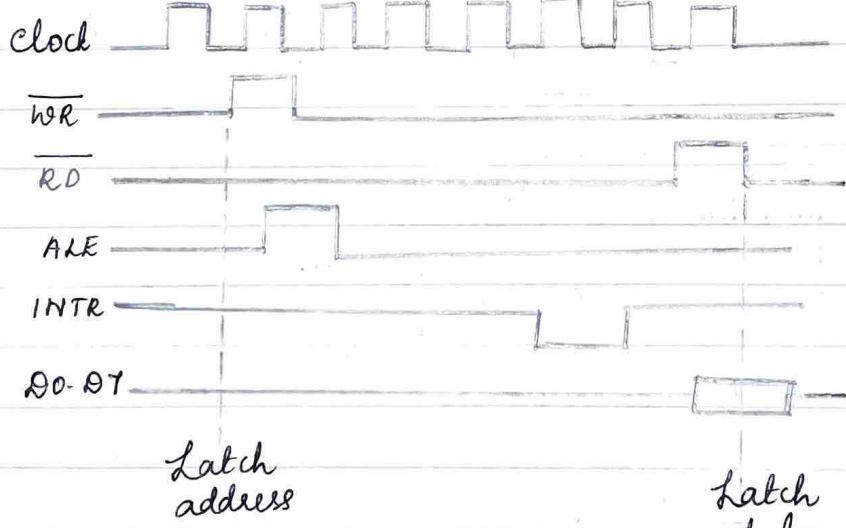


steps to interface ADC 0808 to 8051

- Select an analog channel by providing bits to A, B, and C addresses

- ii) Activate ALE pin
- iii) Activate SC (start conversion) by L-H pulse.
- iv) Monitor EOC (end of conversion) to see whether conversion is finished
- v) Delay size depends on the external clock connected to clock pin
- vi) Activate OE (output enable) to read data out of the ADC chip.

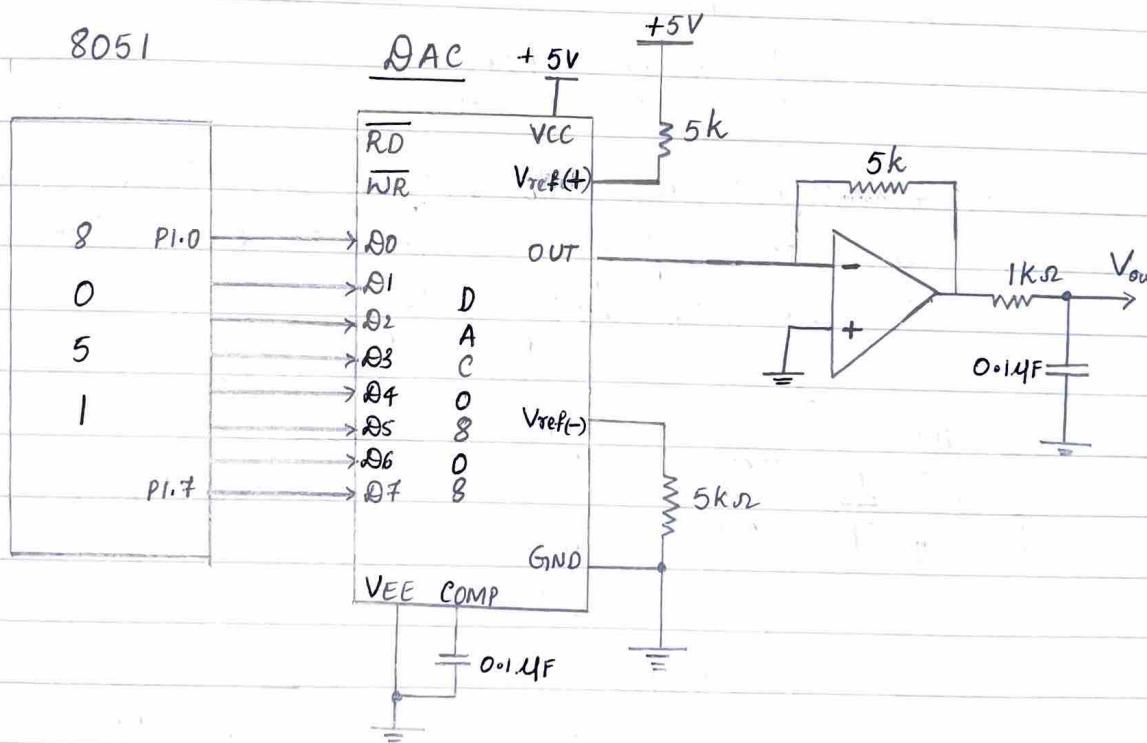* 6) Explain with a diagram the interfacing of DAC 0808 with 8051 chip



DAC 0808 interfacing with 8051

- DAC - Digital to analog converter is a device widely used to convert digital pulses to analog signals.
- In DAC 0808 the digital inputs are converted to

(I_{out}) and by connecting a resistor to the I_{out} pin we convert the result to voltage.


- Total current I_{out} is given by,

$$I_{out} = I_{ref} \left(\frac{D_7}{2} + \frac{D_6}{4} + \frac{D_5}{8} + \frac{D_4}{16} + \frac{D_3}{32} + \frac{D_2}{64} + \frac{D_1}{128} + \frac{D_0}{256} \right)$$

where D_0 is the LSB & D_7 is the MSB, I_{ref} is the input current to pin 14. Generally I_{ref} is 2mA.

- I_{ref} is isolated by connecting it to an op-amp such as the 741 IC. with $R_f = 5k\Omega$ for feed back resistor
- Assuming $R = 5k\Omega$, by changing the binary input the op voltage changes.

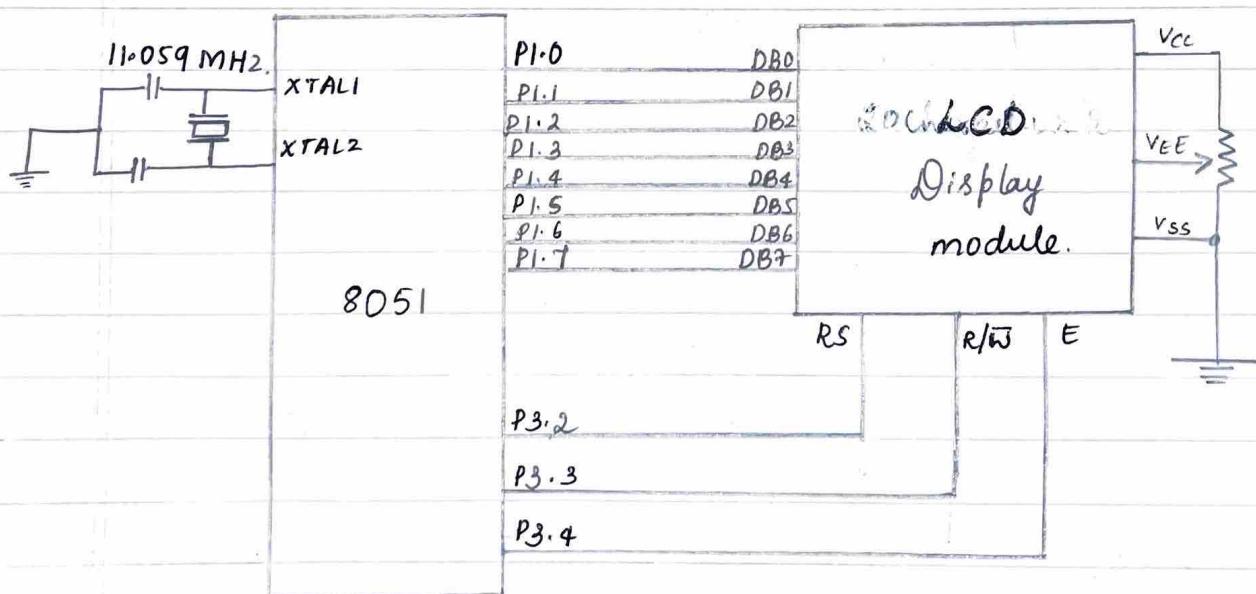- 7) Interface an LCD display to 8051 and write an 8051 C program to send letters 'M', 'D' & 'L' to LCD using delays.



Interfacing LCD with 8051

Program:-

```

#include <reg51.h>
sfr lcd = 0x90;
sbit RS = P2^10;
sbit RW = P2^11;
sbit EN = P2^12;
void main ()
{
    lcdm(0x38);
    msdelay(250);
    lcdm(0x0E);
    msdelay(250);
    lcdm(0x01);
    msdelay(250);
    lcdm(0x06);
    msdelay(250);
    lcdm(0x86);
    msdelay(250);
    data('M');
    msdelay(250);
    data('0');
    msdelay(250);
    data('E');
}

```

Void lcdm (unsigned char)

{

```

lcd = value;

```

RS = 0;

RW = 0;

EN = 1;

msdelay(1);

EN = 0;

}

return;

Void data (unsigned char value).

}

lcd = value;

RS = 1;

RW = 0;

EN = 1;

MS delay (1);

EN = 0;

return;

}

void ms delay (unsigned int itime)

{

unsigned int i, j;

for (i=0; i< itime; i++)

for (j=0; j< itime; j++)

}

8 * Write 8051-c program to display message "good
luck" in LCD interfacing (Same as previous
program)

9 * Interface LCD & write a program to send
"WELCOME" to LCD display using delays

ALP-LCD

Org 0000h

mov 81h, #30h

mov A, #38h

lcall loop

mov A, #0Eh

lcall loop

mov A, #01;

L call loop.

mov A, #06.

L call loop

mov A, #86

L call loop.

mov A, '#W'

L call display

mov A, '#E'

L call display

mov A, '#L'

L call display

mov A, '#C'

L call display

mov A, '#O'

L call display

mov A, '#M'

L call display

mov A, '#E'

Sjmp here

loop: L call up

mov P1, A.

clr P3.2

clr P3.3

clr P3.4

Setb P3.4

up: clr P3.4

clr P3.2

mov P1, #0ffh.

read: Setb P3.3

Setb P3.4

JB P1.7, read.

clr P3.4

display: L call ready

mov P1, A.

Setb P3.2.

clr P3.3.

Setb P3.4

clr P3.4.


RET.

* Pin description for LCD.

- 1) V_{SS} - Ground pin.
- 2) V_{CC} - +5V power supply
- 3) V_{EE} - Power supply to control contrast.
- 4) RS - Register select I/p pin
 $RS = 0 \rightarrow$ data register is selected

$RS = 0 \rightarrow$ commonal register is selected.

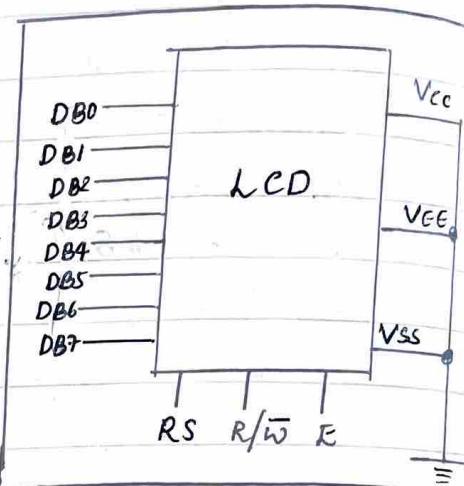- 5) R/W - Input pin which allows the user to write data to the LCD & read data from LCD.
- 6) E - This input pin is used by LCD to latch information
- 7) DB₀-DB₇ - I/O pins - These 8-bit data bus pins are used to send or to read information for LCD.



10 * Write 8051 ALP to rotate a stepper motor 64° in clockwise direction. The motor step angle is 2° . Use 4 step sequence & draw the schematic diagram. step per revolution = 180° . no of rotor tooth = 45. movement per 4 step sequence = 8° .


Given:- Step angle = 2°

one revolution = 360°

movement per 4 step = $4 \times 2^\circ = 8^\circ$

steps per revolution = $\frac{360^\circ}{8^\circ} = 45$

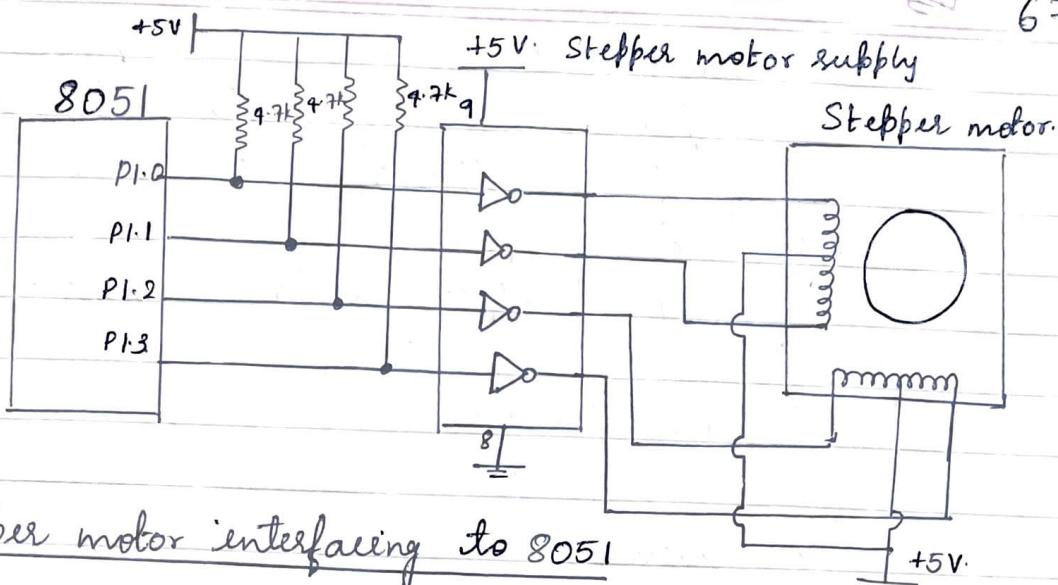To rotate motor $64^\circ = \frac{64}{8} = 8$ (counts)



Stepper motor interfacing to 8051

AJP

org 0000h

MOV R2, #08h

up: MOV A, #01h

MOV P2, A

A call delay

MOV A, #02h

MOV P2, A

A call delay

MOV A, #04h

MOV P2, A

A call delay

MOV A, #08h

MOV P2, A

A call delay

DJNZ R2, up.

MOV R3, #100

here: MOV R4, #255

loop: DJNZ R4, loop

DJNZ R3, here

End.

include < reg51.h >

void delay (unsigned int);

void main (void)

{

unsigned char x;

for (x=0; x<8; x++)

{

P2 = 0x00;

delay (1);

P2 = 0x02;

delay (1);

P2 = 0x04;

delay (1);

P2 = 0x08;

delay (1);

{

void delay (unsigned int, time)

{

unsigned int i, j;

for (i=0; i<200; i++)

{

for (j=0; j<1275; j++)

11 * A switch is connected to pin P2.7 write a C program to monitor the status of SW & perform the following

- 1) If SW=0 stepper motor rotates in clockwise
- 2) If SW=1 stepper motor rotates in counter clockwise

```
#include <reg51.h>
```

```
8bit SW = P2^7;
```

```
void main (void)
```

```
{
```

```
SW = 1;
```

```
while(1)
```

```
{
```

```
if (SW == 0)
```

```
{
```

```
P1 = 0x66;
```

```
MS delay();
```

```
P1 = 0xcc;
```

```
MS delay();
```

```
P1 = 0x99;
```

```
MS delay();
```

```
P1 = 0x33;
```

```
MS delay();
```

```
else
```

```
{
```

```
P1 = 0x66;
```

```
MS delay();
```

```
P1 = 0x33;
```

```
MS delay();
```

```
P1 = 0x99;
```

```
MS delay();
```

```
P1 = 0xcc;
```

```
MS delay();
```

```
{
```

```
void msDelay (unsigned int time)
```

```
{
```

```
unsigned int i, j;
```

```
for (i = 0; i < time; i++)
```

```
for (j = 0; j < 1275; j++)
```

```
{
```

12 * Consider 8-bit ADC Assume $V_{ref} = 5V$ Calculate 8-bit digital output when $V_{in} = 3V$.

$$V_{ref} = 5V$$

$$V_{in} = 3V$$

$$h \& KT, D_{out} = \frac{V_{in}}{\text{Step size}}$$

$$\text{Step size} = \frac{V_{ref}}{256} = \frac{5}{256} = \underline{\underline{19.5mV}}$$

$$D_{out} = \frac{3}{19.5m} = \underline{\underline{153.6A}} \simeq \underline{\underline{154A}}$$

$$\therefore D_{out} = \underline{\underline{9Ah}}$$

13 * for a given ADC 0808 we have $V_{ref} = 2.56V$
calculate $D_0 - D_7$ output (D_{out}) if analog input is 1.7V

$$V_{ref} = 2.56V$$

$$V_{in} = 1.7V$$

$$h \& KT, D_{out} = \frac{V_{in}}{\text{Step size}}$$

$$\text{Step size} = \frac{V_{ref}}{256} = \frac{2.56}{256} = 10mA$$

$$\therefore D_{out} = \frac{1.7}{10mA} = \underline{\underline{170}} \quad (\text{in decimal})$$

$$\therefore D_7 - D_0 \Rightarrow \underline{\underline{10101010}} \quad (\text{binary})$$

Q * Explain about stepper motor interface with diagram & also write a C program if motor takes 90° steps to complete one revolution & show the calculation.

$$\Rightarrow \text{Total no of steps} = 90 / \text{revolution}$$

$$\Rightarrow \text{Step Angle} = \frac{360^\circ}{\text{total no of steps / revolution}}$$

$$\Rightarrow \text{Step Angle} = \frac{360}{90} = 4^\circ$$

$$\Rightarrow \text{One revolution} = \underline{\underline{360^\circ}}$$

$$\Rightarrow \text{Steps per 4 revolution} = 4 \times 4 = \underline{\underline{16^\circ}} \text{ (sequence)}$$

$$\Rightarrow \text{No of counts} = \frac{\text{total steps}}{\text{sequences}} = \frac{90}{16} = \underline{\underline{6 \text{ count}}}$$

#include <reg51.h>

void ms_delay (unsigned int);

Void delay (void).

{

 unsigned char x;

 for (x=0; x<5; x++);

}

(Same previous program) Q NO - 10

15. Write a program to produce square wave & triangular wave using DAC interface

Square wave

```

Org 0000h
mov SP, #08h.

repeat: mov P1, #0ffh
        l call delay.
        mov P1, #00h
        l call delay
        djmp repeat

delay: mov R0, #0ffh
back: djnz R0, back.
        ret.
    
```

Triangular wave

```

Org 0000h
mov SP, #08h
mov R0, #00h

repeat: mov P1, R0.
        inc R0.
        cjne R0, #0ffh, repeat
        djnz R0, loop.
        djmp repeat.
    
```

16. Explain internal architecture of AD0804 also draw its timing diagram.

Features

<u>CS</u>	1	20	Vcc
<u>RD</u>	2	19	Clk (out)
<u>WR</u>	3	18	DB0
(in) <u>clk</u>	4	ADC	17 - DB1
<u>INTR</u>	5	0804	16 - DB2
<u>INT</u>	6		15 - DB3
<u>IN</u> -	7		14 - DB4
(Analog) <u>GND</u>	8		13 - DB5
<u>REF</u>	9		12 - DB6
(Digital) <u>GND</u>	10		11 - DB7

- * 8 bit successive ADC.
- * Conversion time 100 μs
- * Access time 135 ns.
- * It has on chip clock generator
- * It operates of 5V power supply

Timing diagram to convert analog data to digital

